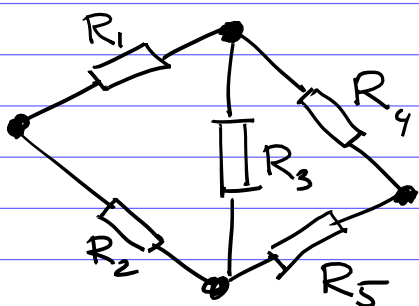


Electrical Networks

$G = (V, E)$ graph on vertex set $V = [n]$.

We'll view edges of G as resistors.



Edge weights = Conductivities = $\frac{1}{\text{resistances}}$

Let's fix directions of edges of G .

So, G is a digraph.

Remark.

We can pick edge directions in any way. (Like we did in the proof of undirected M.T.T. based on the Cauchy-Binet formula.)

We need edge directions to decide which directions of current should be regarded positive or negative.

Directed M.T.T., arborescences, etc depend on a directed graph in an essential way.

But here edge directions are needed just for notational purposes. The construction will not change if we reverse directions of some edges.

Any (directed) edge e in G has

- resistance $R_e \in \mathbb{R}_{>0}$.
- current $I_e \in \mathbb{R}$
- voltage (or potential difference)
 $V_e \in \mathbb{R}$.

Remark. If we reverse the direction of edge e , then resistance remains the same, but the current & voltage reverse the sign:

$$R_{-e} = R_e$$

$$I_{-e} = -I_e$$

$$V_{-e} = -V_e$$


Typically, we'll assume that the graph G and resistances R_e are given. And we'll try to calculate the currents I_e and voltages V_e using the law of electricity.

Laws of Electricity

1st Kirchhoff's Law:

For any vertex $v \in V$,
the sum of in-currents =
= the sum of out-currents:
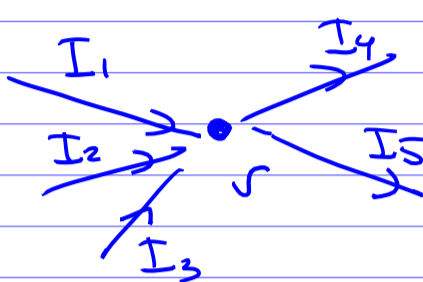
$$\sum_{e \rightarrow v} I_e = \sum_{v \rightarrow e'} I_{e'}$$




$$I_1 + I_2 + I_3 = I_4 + I_5$$

2nd Kirchhoff's Law:

For any cycle C in G
with edges e_1, e_2, \dots, e_m the
signed sum of voltages
of e_i 's is zero:

$\pm V_{e_1} \pm V_{e_2} \pm \dots \pm V_{e_m} = 0$,
where the sign is "+" if
the direction of edge e_i agrees
with the orientation of C ,
and "-" if not.

Example

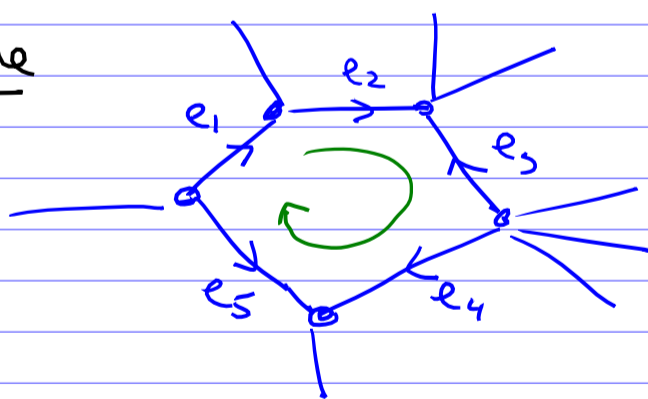

$$V_{e_1} + V_{e_2} - V_{e_3} + V_{e_4} - V_{e_5} = 0$$

Lemma 2nd Kirchhoff's Law is
equivalent to existence of
function $U: \{\text{vertices of } G\} \rightarrow \mathbb{R}$
such that, for any edge

$$e: u \rightarrow v,$$

$$V_e = U_v - U_u.$$


Such function U is called the
potential function.

Ohm's Law. For any edge e ,

$$V_e = I_e \cdot R_e.$$

These 3 laws determine everything we need to know about an electrical network.

A typical problem

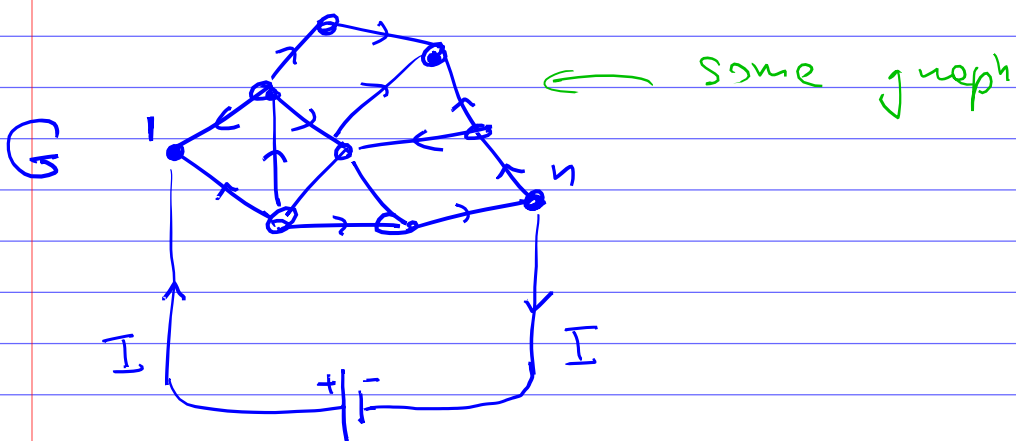

battery connected to the vertices 1 and n .

Known:

- graph G
- resistances R_e of all edges in G
- the voltage of the battery

$$U_1 - U_n$$

Find: All currents and voltages of edges in G .

Let's express electrical laws in matrix form.


We'll express everything using the potential function $\mathcal{V} \mapsto U_{\mathcal{V}}$ (not the voltages

$$V_e = U_{\mathcal{V}} - U_u \quad \text{for } \begin{array}{c} e \\ \xrightarrow{\quad} \\ u \quad \mathcal{V} \end{array}$$

So 2nd Kirchhoff's law will hold automatically.

$$\text{Ohm's law: } I_e = \frac{V_e}{R_e} = \frac{U_{\mathcal{V}} - U_u}{R_e}$$

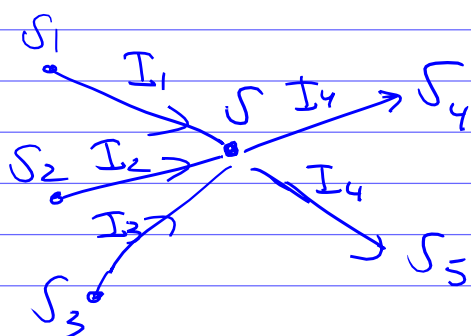Let's express the 1st Kirchhoff's law using the potential:



$$\underbrace{I_1 + I_2 + I_3}_{\text{in-current to } \mathcal{V}} = \underbrace{I_4 + I_5}_{\text{out-current from } \mathcal{V}}$$


The same equation in terms of potential:

$$I_1 \frac{U_{\mathcal{V}} - U_{S_1}}{R_1} + \overset{I_2}{\swarrow} \frac{U_{\mathcal{V}} - U_{S_2}}{R_2} + \frac{U_{\mathcal{V}} - U_{S_3}}{R_3} \overset{I_3}{\swarrow} =$$

$$= \frac{U_{S_4} - U_{\mathcal{V}}}{R_4} \overset{I_4}{\swarrow} + \frac{U_{S_5} - U_{\mathcal{V}}}{R_5} \overset{I_5}{\swarrow}$$

$$\text{or } \sum_i \frac{U_{\mathcal{V}} - U_{S_i}}{R_i} = 0$$

In general, we have:

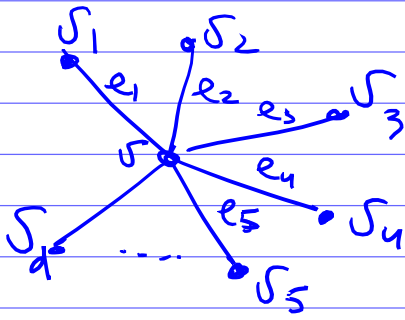


For any vertex $v \in V$ connected to vertices v_1, \dots, v_d by edges e_1, \dots, e_d with resistances R_1, \dots, R_d we have

$$\left(\frac{1}{R_1} + \dots + \frac{1}{R_d} \right) U_v - \sum_{i=1}^d \frac{1}{R_i} U_{v_i} =$$

$$= \begin{cases} 0 & i \neq 1, n \\ -I & i = 1 \\ I & i = n \end{cases}$$

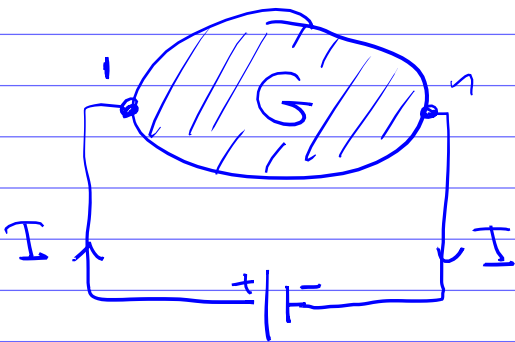Here we assume that we connect a battery to vertices 1 and n , and $I = I_{\text{battery}}$ is the current through the battery:



So for vertex 1 we have additional in-current I from the battery, and for vertex n we have additional out-current I .

Define the Kirchoff's matrix

$K = (K_{ij})$ as the $n \times n$ matrix

$$K_{ij} = \begin{cases} \sum_{\substack{e \text{ edge} \\ \text{adjacent to } i}} C_e & \text{if } i=j \\ -\sum_{\substack{e: \text{ edge} \\ \text{between } i \& j}} C_e & \text{if } i \neq j \end{cases}$$

where $C_e := \frac{1}{R_e}$ are the

conductivities of edges e .

Remark. The Kirchoff's matrix is exactly the weighted Laplacian matrix for the undirected graph G with edge weights C_e .

This is why we earlier said that the Laplacian matrix is the same thing as the Kirchoff's matrix.

Let $\vec{U} = \begin{bmatrix} U_1 \\ \vdots \\ U_n \end{bmatrix}$ be the

vector of potentials.

(Its entries are the potentials U_s of all vertices $s=1, \dots, n$.)

Now all 3 laws of electricity can be expressed by a single equation:

$$(*) \quad K \cdot \vec{U} = \begin{bmatrix} -I \\ 0 \\ \vdots \\ 0 \\ I \end{bmatrix}$$

This is a system of n linear equations for n unknowns (potentials) U_1, \dots, U_n .

But we have a little problem: the matrix K is not invertible, i.e. $\det(K) = 0$.

How do we solve the above system of linear equations?

Actually, this is not really surprising because (*) does not have a unique solution.

The potential function is defined up to a constant:

If $\begin{bmatrix} U_1 \\ \vdots \\ U_n \end{bmatrix}$ is a solution of (*),


then $\begin{bmatrix} U_1 + a \\ U_2 + a \\ \vdots \\ U_n + a \end{bmatrix}$ is also a solution of (*).

Indeed, the law of electricity are expressed in terms of potential differences $U_5 - U_4$, i.e. voltages.

(Only potential differences $U_5 - U_4$ have physical meaning.)

We can fix this ambiguity by requiring that $U_n = 0$.

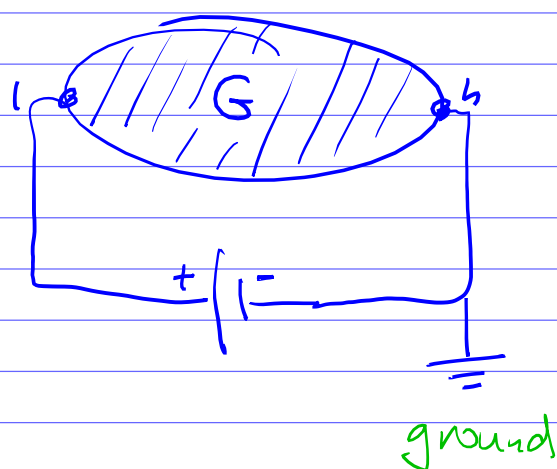In other words we can "ground" vertex n .



Let \tilde{K} be the reduced Kirchhoff's matrix obtained from K by removing the last row & the last column.

Then $(*) \Leftrightarrow$

$$(**) \quad \tilde{K} \cdot \begin{bmatrix} U_1 \\ \vdots \\ U_{n-1} \end{bmatrix} = \begin{bmatrix} -I \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

$(n-1) \times (n-1)$
matrix

Now \tilde{K} is an invertible matrix (if G is a connected graph) and $(**)$ has a unique solution.

What is I ?

We know the voltage of the battery $V_{\text{bat}} = U_1 - U_n = U_1 - 0$. But we don't know the current I through the battery.

Here is how to fix this:


- Solve $(**)$ for $I = 1$ (or for any I).

- Rescale the solution


$(U_1, \dots, U_{n-1})^T$ so that

$U_1 - 0$ becomes the given voltage V_{battery} of the battery.

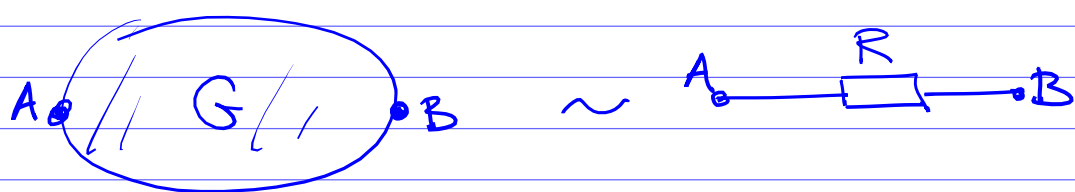The whole graph G acts as a single resistor between two marked vertices A & B .
 (In above construction $A=1$ & $B=n$)



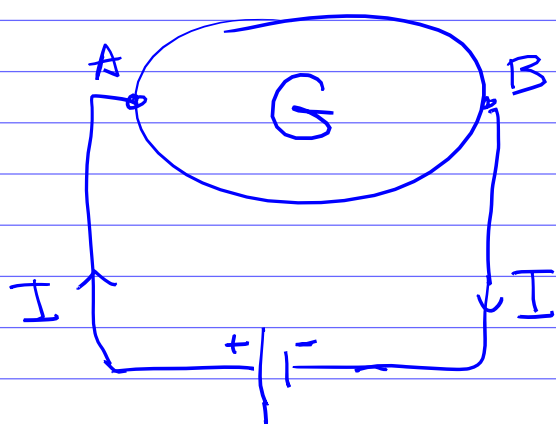How to find the resistance $R_{AB}(G)$ if we know resistances of all edges in G ?



By Ohm's Law

$$R_{AB}(G) = \frac{U_A - U_B}{I}$$

Solving (***) by Cramer's rule

we deduce

$$R_{AB}(G) = \frac{\det \tilde{K}}{\det K}$$

matrix obtained from K by removing 2 rows & two columns with labels A & B

Both numerator & denominator can be interpreted using (weighted) matrix tree theorem.

Theorem Let G be

a weighted graph with
edge weights $C_e = \frac{1}{R_e}$



and two marked vertices A & B .

Let G' be the graph
obtained from G by
gluing vertices A & B into
a single vertex. Then

$$R_{AB}(G) = \frac{\sum_{T \text{ spanning tree of } G'} \text{weight}(T)}{\sum_{T \text{ spanning tree of } G} \text{weight}(T)}$$

Examples.

Series connection

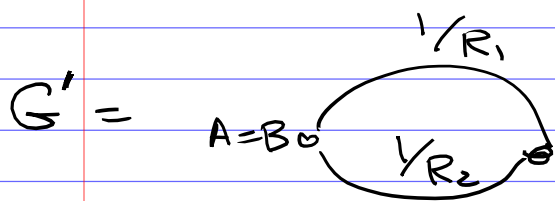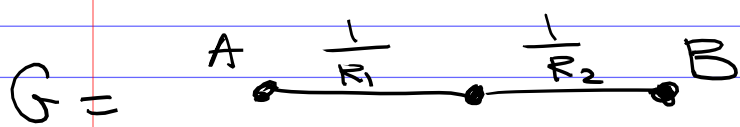

2 spanning trees of G'



$$R_{AB}(G) = \frac{\frac{1}{R_1} + \frac{1}{R_2}}{\frac{1}{R_1} \cdot \frac{1}{R_2}}$$

1 spanning tree of G

$$= R_1 + R_2.$$

For a series connection, we
need to add resistances

Parallel connection

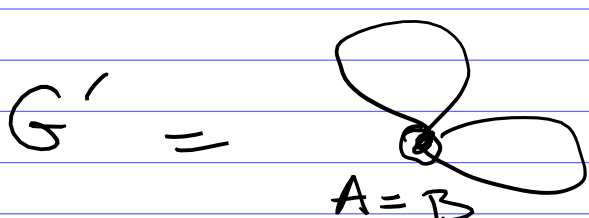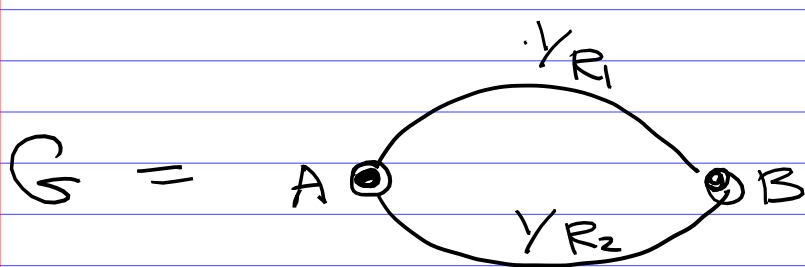



$$R_{AB}(G) = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

1 empty spanning tree of G'

2 spanning trees of G

For a series connection inverses of resistances add.

Another example

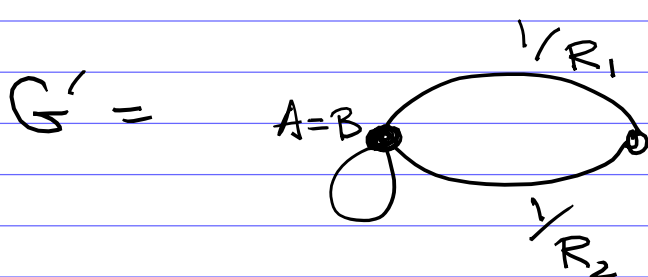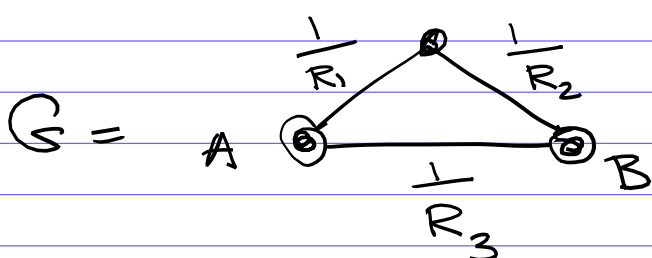


$$R_{AB} = \frac{\frac{1}{R_1} + \frac{1}{R_2}}{\frac{1}{R_1} \cdot \frac{1}{R_2} + \frac{1}{R_1} \cdot \frac{1}{R_3} + \frac{1}{R_2} \cdot \frac{1}{R_3}}$$


2 spanning trees of G'

3 spanning trees of G

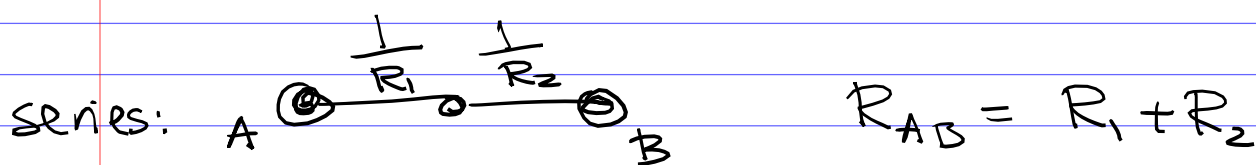Let's try to get the same result by first doing a series connection & then a parallel connection:



$$R_{AB} = R_1 + R_2$$

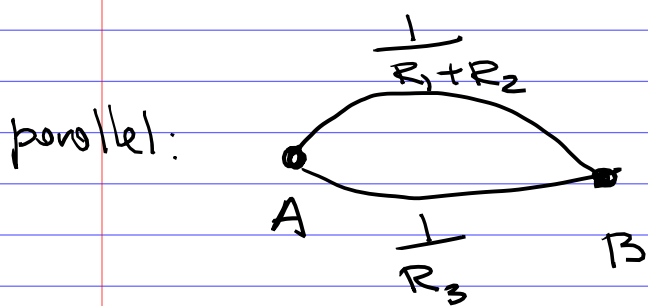


$$R_{AB}(G) = \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{R_3}}$$

$$= \frac{R_1 + R_2}{1 + \frac{R_1}{R_3} + \frac{R_2}{R_3}}$$


$$= \text{same expression as above.}$$

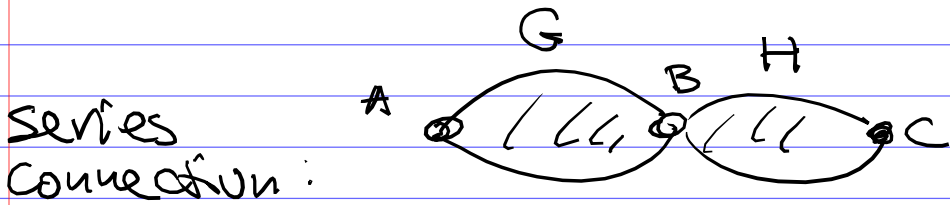In general, for any two connected graphs G & H with edge weights $= \frac{1}{R_e}$ and 2 marked vertices in each graph, we have



$$R_{AC}(G \text{--} H) = R_{AB}(G) + R_{BC}(H)$$

parallel connection:

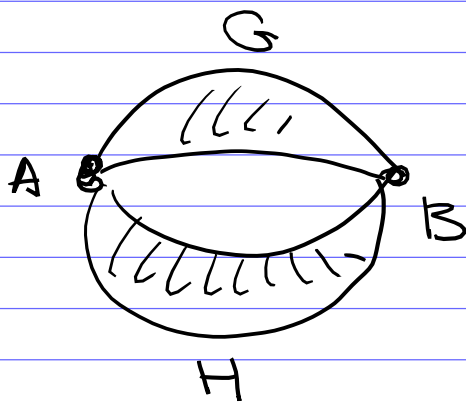


$$R_{AB}(G \parallel H)$$

$$= \frac{1}{\frac{1}{R_{AB}(G)} + \frac{1}{R_{AB}(H)}}$$

Exercise. Interpret & prove both formulas using spanning trees.

Weighted graphs that can be constructed from single edges by a sequence of series & parallel connections are called series-parallel networks:

Example

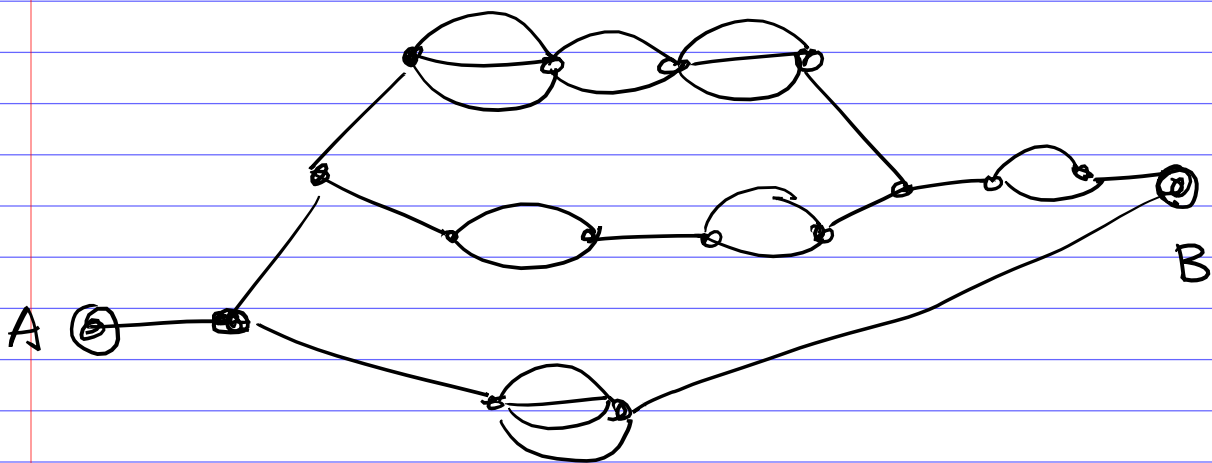


a series-parallel network

It is easy to calculate resistances of such networks using above formulas:

series: $R_1 + R_2$


parallel: $\left((R_1)^{-1} + (R_2)^{-1} \right)^{-1}$

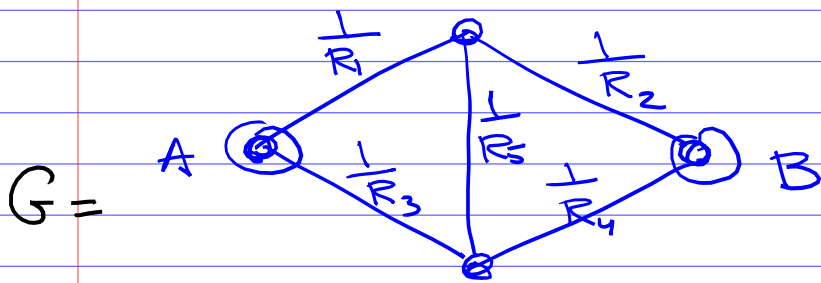Here is the smallest example of a graph that cannot be obtained by series-parallel connections:



Wheatstone bridge

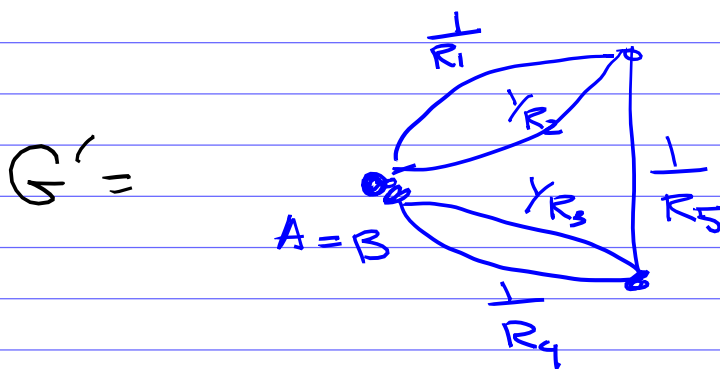We can calculate the resistance $R_{AB}(G)$ using spanning trees



$R_{AB}(G) =$ 8 spanning trees of G'

$$= \frac{\left(\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) \cdot \frac{1}{R_5} + \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \left(\frac{1}{R_3} + \frac{1}{R_4} \right) \right)}{\left(\frac{1}{R_1} \cdot \frac{1}{R_2} \cdot \frac{1}{R_3} + \frac{1}{R_1} \cdot \frac{1}{R_2} \cdot \frac{1}{R_4} + \frac{1}{R_1} \cdot \frac{1}{R_3} \cdot \frac{1}{R_4} + \frac{1}{R_2} \cdot \frac{1}{R_3} \cdot \frac{1}{R_4} + \left(\frac{1}{R_1} + \frac{1}{R_3} \right) \cdot \left(\frac{1}{R_2} + \frac{1}{R_4} \right) \cdot \frac{1}{R_5} \right)}$$

8 spanning trees of G .